

University of Bahrain  
College of Information Technology  
Department of Computer Engineering

ITCE 202 section 1

Name:-----

I.D.:-----

**Quiz (9)**

Prepared by: Dr. Hessa Al-Junaid

18<sup>th</sup> December 2012

Time duration: 10 minutes

Complete the following timing diagram for a J-K Flip Flop shown in the figure.

